


OPTICAL RECEIVER KVS7LQD #

TYPICAL PHOTODIODE WILL OUTPUT $\approx 2\text{ nA}$ OF CURRENT AT MAX LIGHT (ASSUMED FROM GENERAL RESEARCH). I'LL USE A TRANS IMPEDANCE AMPLIFIER TO AMPLIFY THE RECEIVED CURRENT WAVEFORM INTO A VOLTAGE WAVEFORM.

I'LL HAVE A $+5\text{V}$ RAIL, THIS CIRCUIT DRIVES INTO A HEADPHONE AMP. TARGET V_O IS 1V . THE TRANSIMPEDANCE IS OUTPUTTING A 4 kHz BANDWIDTH.

SPEC'S

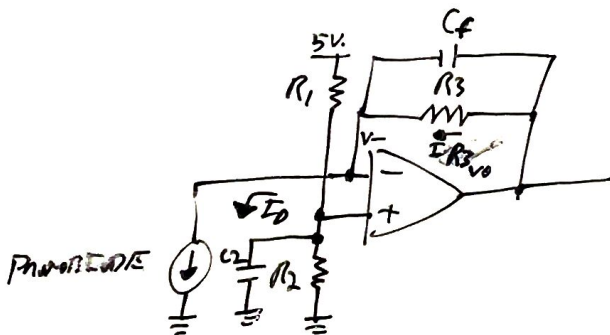$I_{in} = 0.5 - 2\text{ nA} \rightarrow 0.5\text{ nA}$ CHOSEN ARBITRARILLY FOR EMP. JUDGEMENT AS LOWEST SIGNAL
 $V_{OUT} = 1\text{V}_{P-P}$, $V_{OFFSET} \rightarrow$ AN OFFSET OF 1V ALLOWS FOR AUDIO SIGNALS TO NOT SATURATE
 $\text{BW} = 4\text{ kHz}$ NEGATIVE RAIL USING SAME SUPPLY.
 $V_{CC} = 5\text{V}$



- 1) SET R_3 TO OUTPUT $\frac{V_{PP}}{2} = 500\text{ mV}$ AT MAX INPUT PHOTODIODE CURRENT. WITH A 1V OFFSET THIS IS 1.5V MAX

$$I_{R3} = I_0$$

$$V_{R3} = \frac{V_O - V_-}{I_{Dmax}} = \frac{1.5\text{V} - 1\text{V}}{2\text{ nA}} = \frac{0.5\text{V}}{2\text{ nA}} = \boxed{250\text{ k}\Omega} = 299\text{ k}\Omega$$

I WANT TO MAKE THIS VARIABLE BETWEEN 500 nA & 2 nA

$$V_{R3} = \frac{V_O - V_-}{I_{Dmin}} = \frac{1.5\text{V} - 1\text{V}}{500\text{ nA}} = \boxed{1\text{ MEG}\Omega}$$

2) SET FEEDBACK CAPACITOR FOR BAND WIDTH. C_f AND R_3 ARE A SIMPLE RC LOW-PASS FILTER. SET AT R_3 MAX

$$C_f(\text{MEG}) \frac{1}{2 \cdot \pi \cdot R_3 \cdot f_{BW}} = \frac{1}{2 \cdot \pi \cdot 1 \text{ MEG} \cdot 4 \text{ KHZ}} = \boxed{39.8 \text{ PF}}$$

USE 33 PF STD VALUE

$$f_{BW}(\text{USE}) = \boxed{4.82 \text{ KHZ}}$$

$$C_f(250K) = \boxed{159.1 \text{ PF}}$$

USE 33 PF SO THAT f_{BW} IS MINIMUM AT HIGHEST GAIN.

$$f_{BW}(C_f = 33 \text{ PF}) = \frac{1}{2 \pi (250K\Omega) (33 \text{ PF})} = \boxed{19.291 \text{ KHZ}}$$

3) CALCULATE OP-AMP GBW. (USE IN TI SBOA220A)

$$GBW > \frac{C_i + C_f}{2 \pi R_1 C_f^2}$$

$$C_i = (C_j + C_d + C_{cm})$$

C_j = C PHOTODIODE JUNCTION
 C_d = OP-AMP DIFF CAPACITANCE
 C_{cm} = OP-AMP Common mode CAPACITANCE

I'M USING THE OPA322 AS DESCRIBED IN APPNOTE.
IT WORKS FINE FOR ME, OPEN TO IMPROVEMENTS LATER.

$$C_d = 5 \text{ PF}$$

$$C_{cm} = 4 \text{ PF}$$

ON SEMI QSD2030
PHOTODIODE IS ~~WUAM 154005~~ EA3590

$$C_j = 15 \text{ PF}$$

$$C_i = 15 \text{ PF} + 5 \text{ PF} + 4 \text{ PF} = 24 \text{ PF}$$

$$f_{BW}(R_3 = 250K) = 33.3 \text{ KHZ}$$


$$f_{BW}(R_3 = 1 \text{ MEG}) = 8.33 \text{ KHZ}$$

I'M NOT SURE THIS IS TOTALLY CORRECT, EQUATION ASSUMES FIXED f_{BW} . OPA322 = 20MHz... MOVING ON..

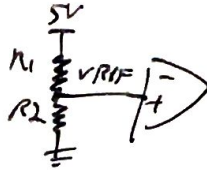4) CALCULATE V_{REF} REFERENCE BEAS = 1V.

$$V_{REF} = 1V$$

$$V_{REF} = \frac{R_2}{R_1 + R_2} \cdot 5V$$



$$(R_1 + R_2) V_{REF} = R_2 \cdot 5V$$

$$\left(\frac{R_1}{R_2} + 1\right) V_{REF} = 5V$$

$$R_1 + R_2 = \frac{5V}{V_{REF}} R_2$$

$$R_1 = \left(\frac{5V}{V_{REF}} - 1\right) R_2$$

ASSUME $R_2 = 10k\Omega$
 $R_1 = 40k\Omega$

$$R_1 = 40.2k\Omega$$

$$R_2 = 10k\Omega$$


$$R_1 = 4.02k\Omega$$

$$R_2 = 1k\Omega$$

5) CALCULATE C_2 @ (9.1nF) STD VALUE

$$f_{P(2)} = \frac{1}{2\pi \cdot C_2 \cdot (R_1 \parallel R_2)} = 21.84 KHz$$

THIS IS A LPF FOR V_{REF}

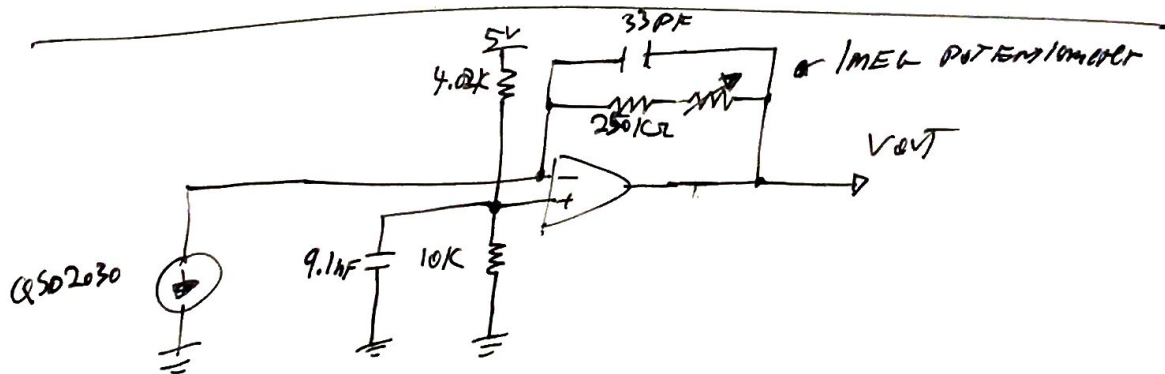

$$f_{TOTAL} = 1.25 MHz \text{ POSSIBLE} = f_{REF} 3.85 KHz$$